
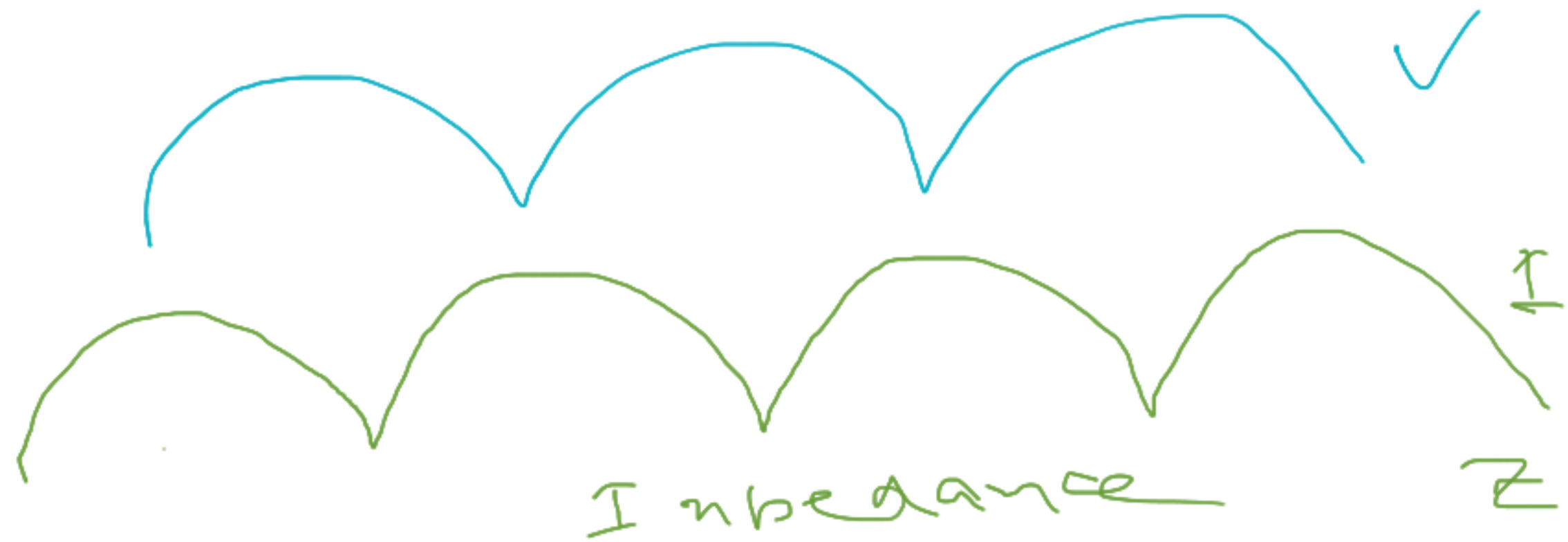


08/04/2021

Input Impedance of a lossless transmission line (Z_{in})

characteristic $Z \rightarrow$ impedance

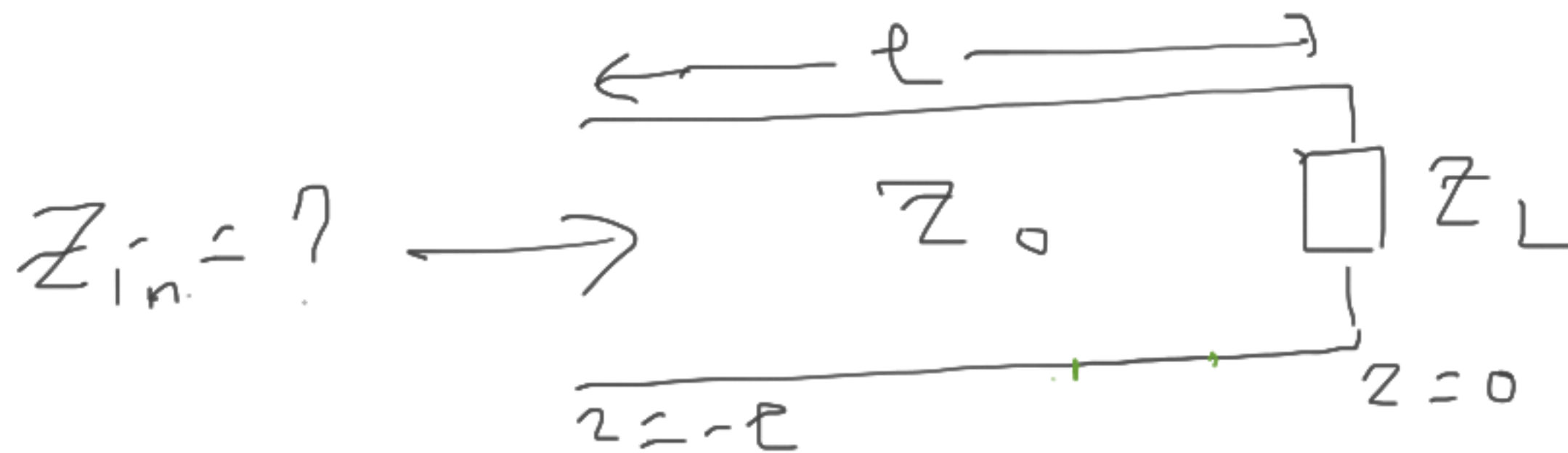Small $Z \rightarrow$ distance length
(3)



with $\gamma = j\beta$ for lossless line (ie, $\alpha = 0$),
we have

$$\textcircled{9} : V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$\textcircled{10} : I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$$

$$\left[\begin{array}{c} - \\ + \end{array} \right] \frac{V_0^\pm}{I_0^\pm} = Z_0 = - \frac{V_0^-}{I_0^-}$$

At distance $z = -l$ from load,
input impedance is given by

$$Z_{in}(z = -l) = \frac{V(z = -l)}{I(z = -l)}$$

$$Z_{in}(z = -l) = Z_0 \cdot \frac{V_0^+ e^{j\beta l} + V_0^- e^{-j\beta l}}{V_0^+ e^{j\beta l} - V_0^- e^{-j\beta l}}$$

(substituted $z = -l$ in (9) & (10) & divide)

$$= Z_0 \cdot \frac{\cancel{V_0^+} (e^{j\beta l} + \frac{V_0^-}{V_0^+} e^{-j\beta l})}{\cancel{V_0^+} (e^{j\beta l} - \frac{V_0^-}{V_0^+} e^{-j\beta l})}$$

$$= Z_0 \cdot \frac{e^{j\beta l} + \Gamma e^{-j\beta l}}{e^{j\beta l} - \Gamma e^{-j\beta l}} \quad \left[\because \Gamma = \frac{V_0^-}{V_0^+} \right]$$

$$\Rightarrow Z_{in} = Z_0 \frac{e^{j\beta l} + \left(\frac{Z_L - Z_0}{Z_L + Z_0}\right)e^{-j\beta l}}{e^{j\beta l} - \left(\frac{Z_L - Z_0}{Z_L + Z_0}\right)e^{+j\beta l}}$$

$$\left[\because \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \right]$$

$$\Rightarrow Z_{in} = Z_0 \cdot \frac{(Z_L + Z_0)e^{j\beta l} + (Z_L - Z_0)e^{-j\beta l}}{(Z_L + Z_0)e^{j\beta l} - (Z_L - Z_0)e^{-j\beta l}}$$

$$\Rightarrow Z_{in} = Z_0 \cdot \frac{Z_L(e^{j\beta l} + e^{-j\beta l}) + Z_0(e^{j\beta l} - e^{-j\beta l})}{Z_L(e^{j\beta l} - e^{-j\beta l}) + Z_0(e^{j\beta l} + e^{-j\beta l})}$$

Recall $e^{j\pi} = \cos \pi + j \sin \pi$ (trigonometric)

$$\Rightarrow e^{j\beta l} = \cos(\beta l) + j \sin(\beta l) \quad \checkmark$$

$$\text{or } e^{-j\beta l} = \cos(\beta l) - j \sin(\beta l) \quad \checkmark$$

Using above,

$$Z_{in} = Z_0 \cdot \frac{Z_L (\cos \beta l) + j Z_0 \sin(\beta l)}{j Z_L \sin(\beta l) + Z_0 \cos(\beta l)}$$

$$\Rightarrow Z_{in} = Z_0 \cdot \frac{Z_L + j Z_0 \frac{\sin(\beta l)}{\cos(\beta l)}}{Z_0 + j Z_L \frac{\sin(\beta l)}{\cos(\beta l)}}$$

$$\Rightarrow Z_{in} = Z_0 \cdot \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)}$$

for a lossless line ($\alpha = 0 \Rightarrow \gamma = \alpha + j\beta = j\beta$) $\beta = \frac{2\pi}{\lambda}$

if line is not lossless, i.e., $\alpha \neq 0$ or $\gamma = \alpha + j\beta$

$$Z_{in} = Z_0 \cdot \frac{Z_L + Z_0 \tanh(\gamma l)}{Z_0 + Z_L \tanh(\gamma l)}$$

hyperbolic tan function

Recall (trigonometry)

$$\sinh(\beta l) = j \sin(\beta l)$$

$$\cosh(\beta l) = \cos(\beta l)$$

$$\tanh(j\beta l) = j \tan(\beta l)$$

Leave
this
slide
(for lossy
line)

hyperbolic
function

$$e^{\pm \gamma l} = \cosh(\gamma l) \pm \sinh(\gamma l)$$

$$Z_{in} = Z_0 \cdot \frac{Z_L + Z_0 \tanh(\gamma l)}{Z_0 + Z_L \tanh(\gamma l)}$$

$\tanh(\gamma l) = \tan(j\beta l)$ for lossless line ($\alpha=0$)
i.e., $\gamma = j\beta$

$$Z_{in} = Z_0 \cdot \frac{Z_L + j Z_0 \tan(\beta l)}{Z_0 + j Z_L \tan(\beta l)}$$

$$Z_{in} = Z_0 \cdot \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \quad \leftarrow \textcircled{A}$$


for lossless line ($\alpha = 0 \Rightarrow \gamma = j\beta$)

Z_{in} depends on Z_L & l

Z_{in} dependency on Z_L

Case-1: $Z_L = 0$ (Short circuit)
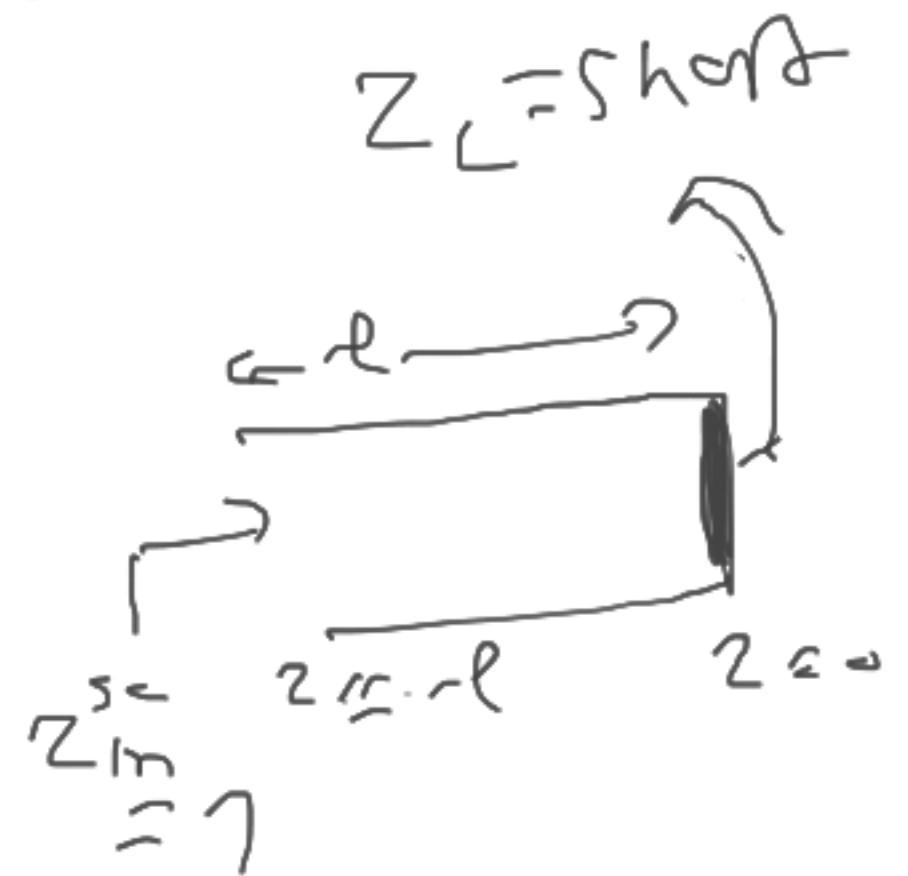
$$\therefore \textcircled{A}: Z_{in}^{sc} = Z_0 \frac{jZ_0 \tan \beta l}{Z_0}$$



input impedance
of a short circuit
(s.c.) line

$\Rightarrow Z_{in}^{sc} = jZ_0 \tan \beta l$

no real part \leftarrow purely reactive line

$$Z_{in}^{sc} = j Z_0 \tan(\beta l)$$

$$\text{At } l=0, \quad Z_{in}^{sc} = 0$$

$$[\because \tan \beta l = 0]$$

$$\text{At } l = \frac{\lambda}{4}, \quad \beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2}$$


$$\Rightarrow \tan \beta l = \tan\left(\frac{\pi}{2}\right) = \infty$$

$$\Rightarrow Z_{in}^{sc} = \infty$$

$$\text{At } l = \frac{\lambda}{2}, \quad \beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = \pi$$

$$\Rightarrow \tan \beta l = \tan(\pi) = 0$$

$$\Rightarrow Z_{in}^{sc} = 0$$

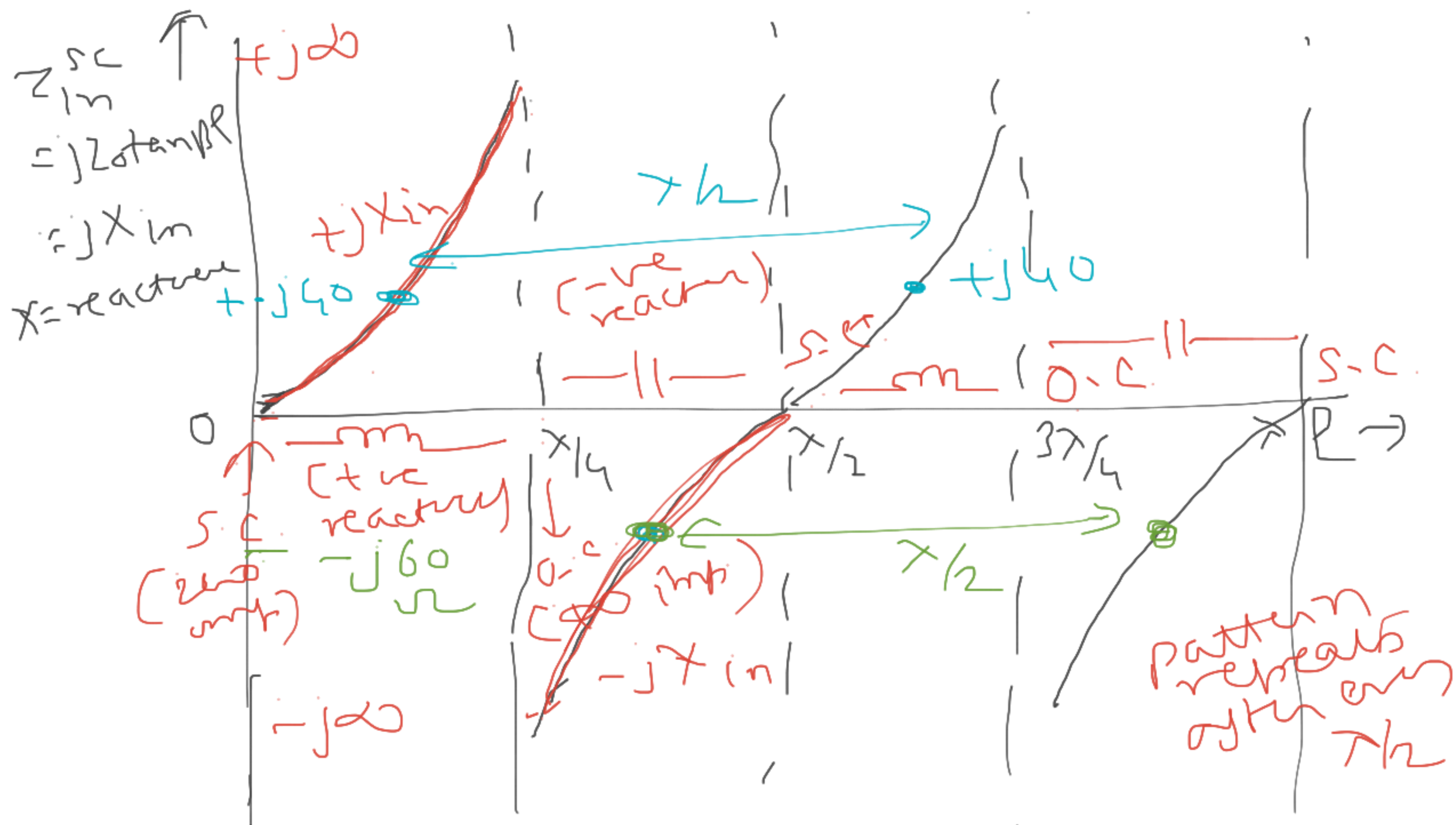

Conclusion.

- 1) An inductor of any value (from $j0$ to $j\infty$)
could be created using a short-circuited
line (i.e., line terminated in $Z_L = 0$)
provided that line length is between

$$0 < l < \lambda/4 \quad \underline{\underline{\text{or}}}$$

$$\frac{\lambda}{2} < l < \frac{3\lambda}{4} \quad \underline{\underline{\text{or}}}$$

multiple of $\lambda/2$

$$\left(+ \frac{n\lambda}{2} \right),$$


$n = 0, 1, 2, \dots$

- 2) S.C. $\frac{\lambda}{4}$ line acts as an inductor (RF choke)

3) S.C. $\xleftarrow{L=\lambda/4}$ O.C.
 O.C. $\xrightarrow{\lambda/4}$ S.C.

4) S.C. $\xrightarrow{\lambda/2}$ S.C.
 O.C. $\xleftarrow{\lambda/2}$ O.C.

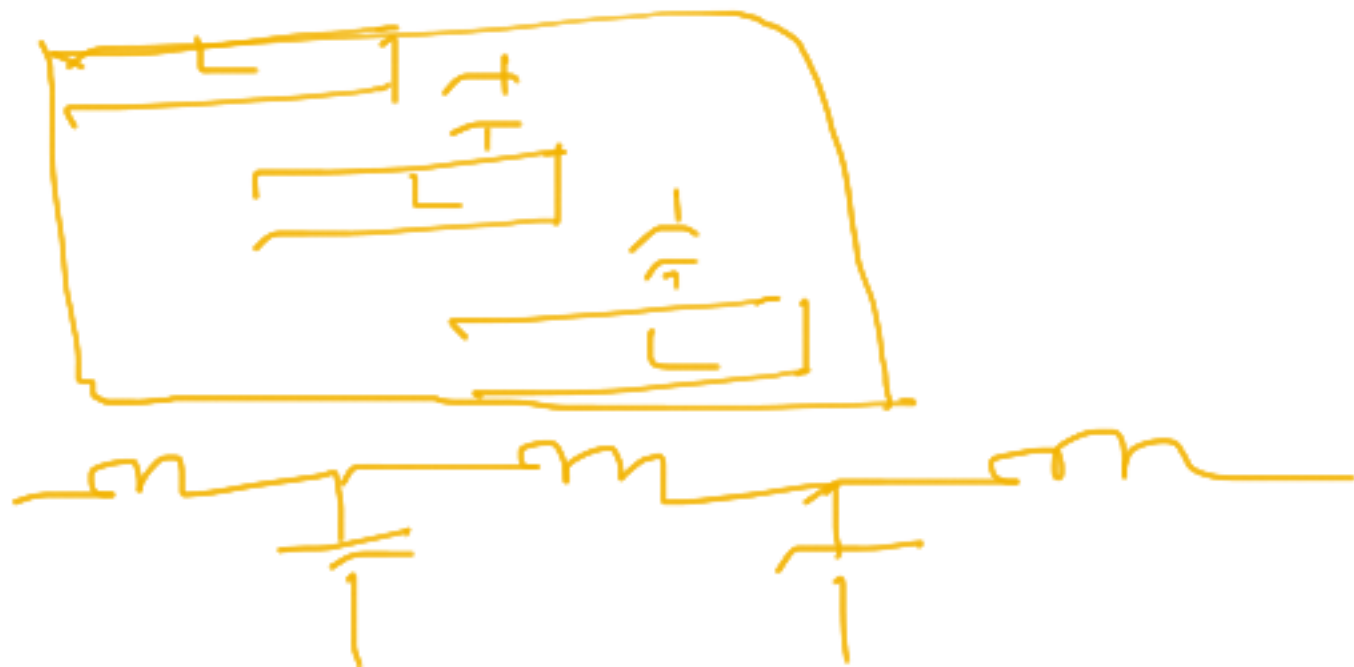3) C $\xleftrightarrow{\lambda/2}$ C
 or
 L



S.C. $\xleftarrow{L=\lambda/4}$ S.C.

