

16/03/2021

Wire

$\overset{L}{\text{mm}} \overset{R}{\text{mm}}$



$$d = \text{mil} = \frac{1}{1000} \text{ inch} = \frac{2.54 \text{ cm}}{1000} = 0.00254 \text{ mm}$$

(diameter)

Resistor : GHz (10^9 Hz)

$\overset{R}{\text{mm}}$ dc or low freq

Start at ac or high freq

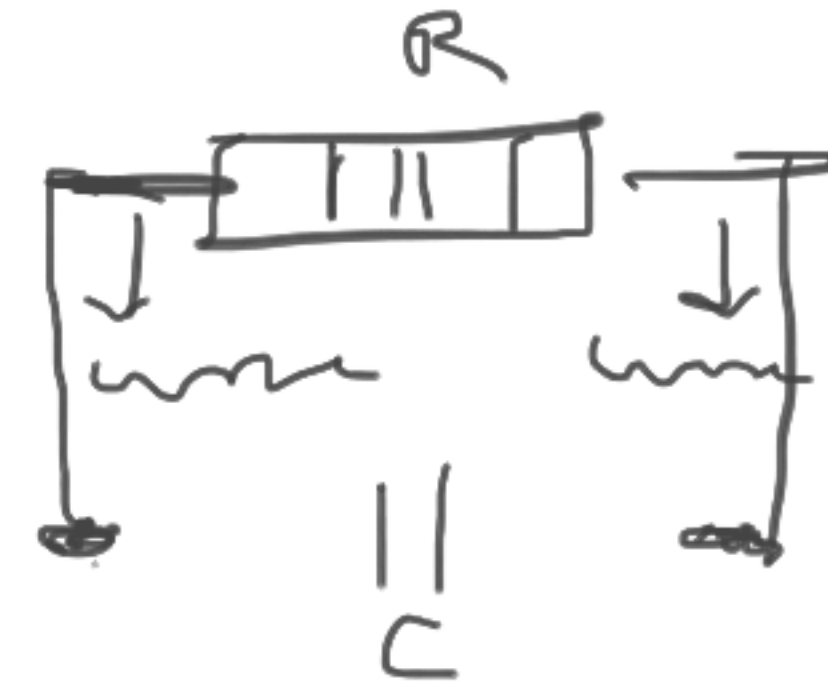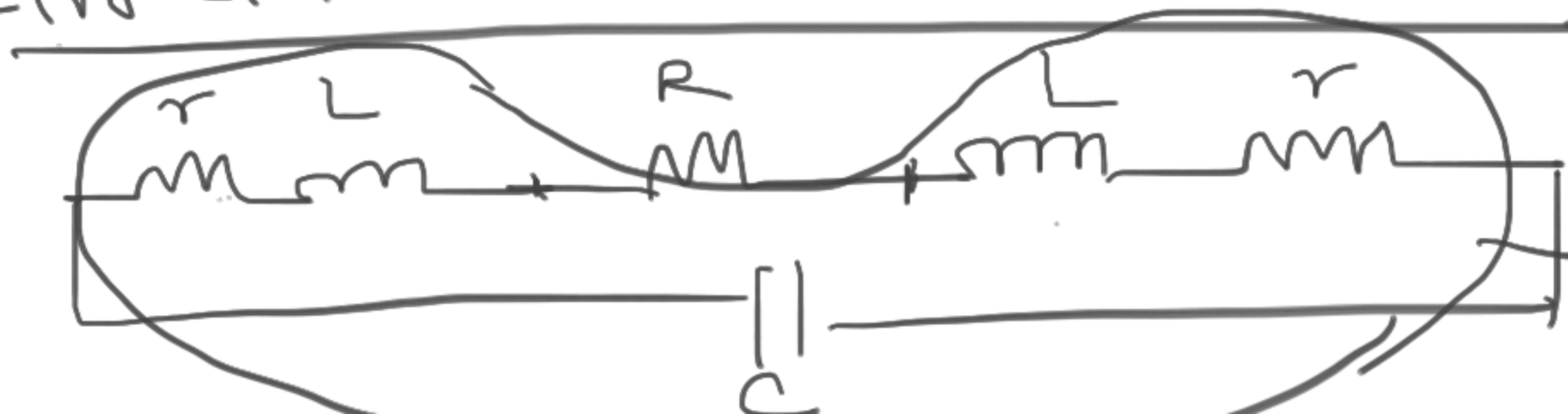


Parasitic or stray elements

Impedance (Ω) : $R, j\omega L, j\omega C$

✓ MFR (Metal Film Resistor) $\rightarrow \frac{1}{4} W$
 $= 0.25 W$
 \downarrow
 Carbon Composite Resistor $= 0.5 W$

Ex //

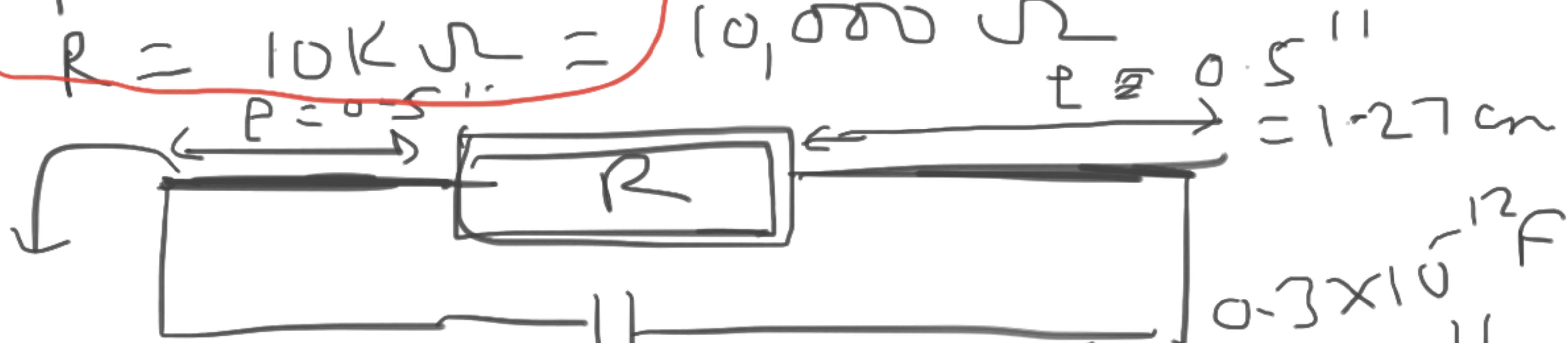$f = 200 \text{ MHz} = 200 \times 10^6 \text{ Hz}$
 $R = 10 K \Omega = 10,000 \Omega$



$d = \text{SWG 14}$
 $= 64 \text{ mils} = 0.1628 \text{ cm} = 64 \times 0.001$
 $(1 \text{ mil} = 0.254 \text{ cm})$
 $C = 0.3 \text{ PF} = 0.3 \times 10^{-12} \text{ F}$

Sol $L = 0.002l \left[2.3 \log \left(\frac{4l}{d} - 0.75 \right) \right]$ μH

no
rate
mege!

$l = \text{length (cm)}$

$d = \text{dia (cm)}$

$\therefore L = 0.002 \times 1.27 \left[2.3 \log \left(\frac{4 \times 1.27}{0.1628} - 0.75 \right) \right]$ μH

$= 0.0087 \mu H$

$= 8.7 \times 10^{-9} H = \underline{\underline{8.7 nH}}$

$C \text{ (provided)} = \underline{\underline{0.3 pF}}$

L presents an eqvt reactance at
200 MHz : (inductive)

$$\underline{X_L = j\omega L = j2\pi fL}$$

$$= 2\pi \times \underbrace{200 \times 10^6} \times \underbrace{8.7 \times 10^{-9}}$$

$$\underline{X_L = j10.93 \Omega}$$


Cap C presents an eqvt reactance at
200 MHz : (capacitive)

$$X_C = \frac{j}{\omega C}$$

$$X_C = \frac{j}{2\pi \times 200 \times 10^6 \times 0.3 \times 10^{-12}}$$


$$\underline{X_C = -j256.3 \Omega}$$

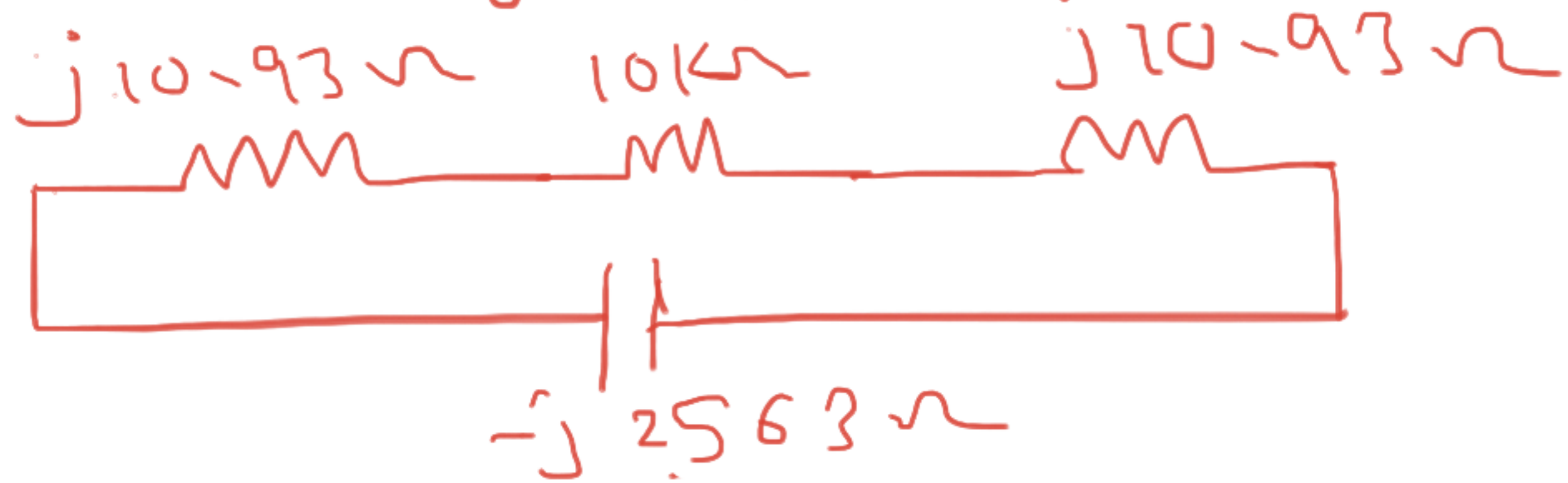\therefore Eqn. ckt of $R (= 10,000 \Omega)$ at 200 MHz :



$j10-93 \Omega \ll 10k\Omega$
 \hookrightarrow neglected

$10k\Omega = R$

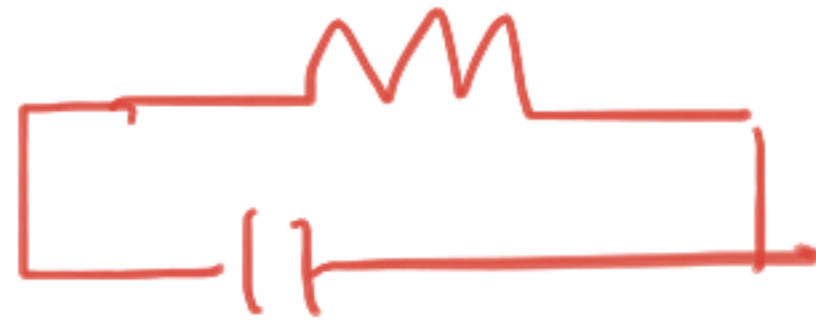

$2563 \Omega = X_c$

$2563 \Omega \parallel 10k\Omega$

$$Z = \frac{RX_c}{\sqrt{R^2 + X_c^2}} = \frac{10K \times 2563}{\sqrt{(10K)^2 + (2563)^2}}$$

$$\underline{Z = 1890 \Omega}$$

→ 10K behaves like $\sim 2K\Omega$ resistor at 200 MHz

$$X_L = X_C$$

$$L, C \quad f_r = \frac{1}{2\pi\sqrt{LC}}$$

Impedance
of
(Ω)

$$R = 10\text{ k}\Omega$$

$$R = 2\text{ k}\Omega$$


Impedance
decreasing
with freq
(capacitive)


Ideal
 R

\rightarrow
Inductive

$f \rightarrow$
(MHz)

1000
(1 kHz)

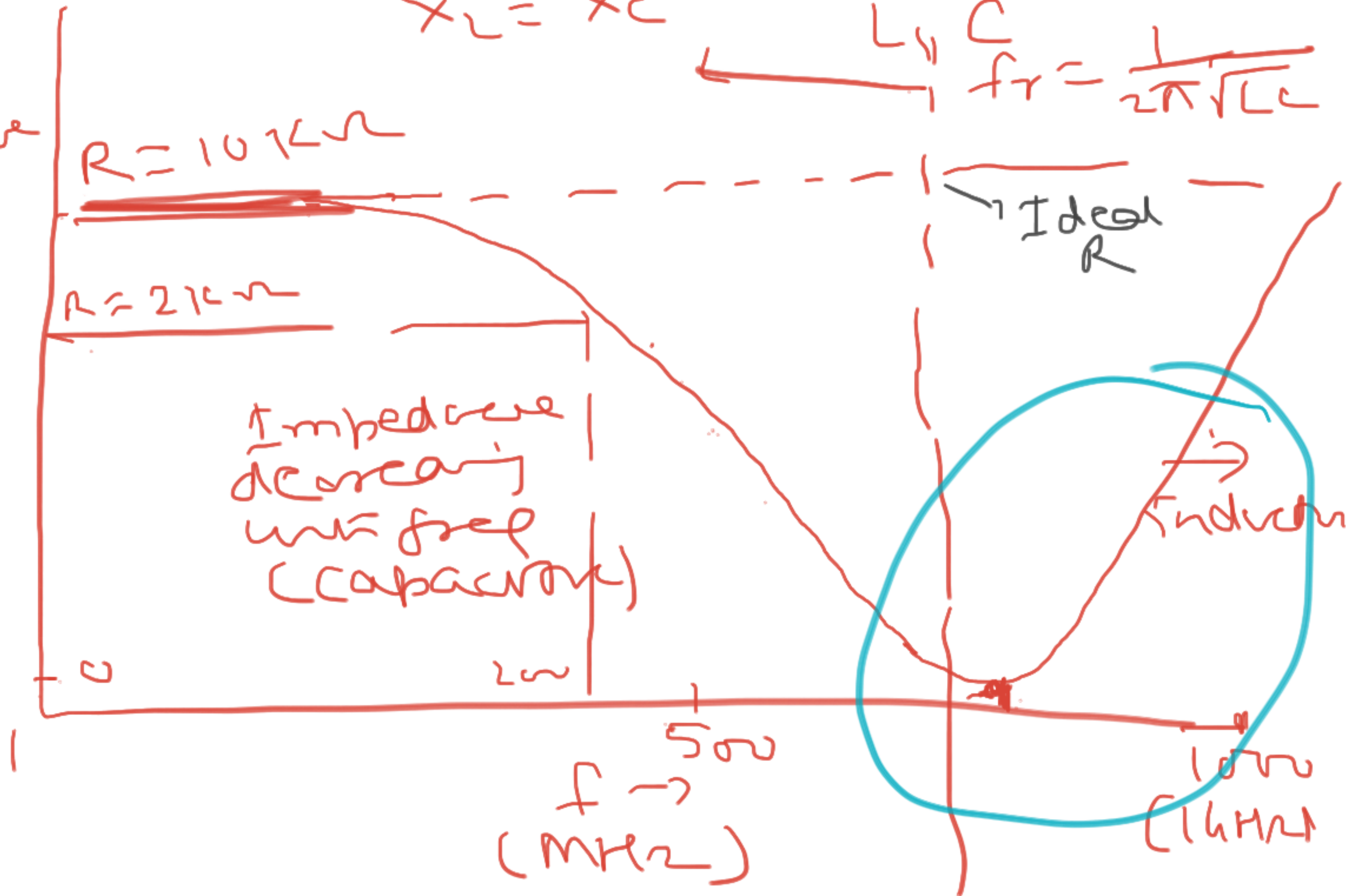

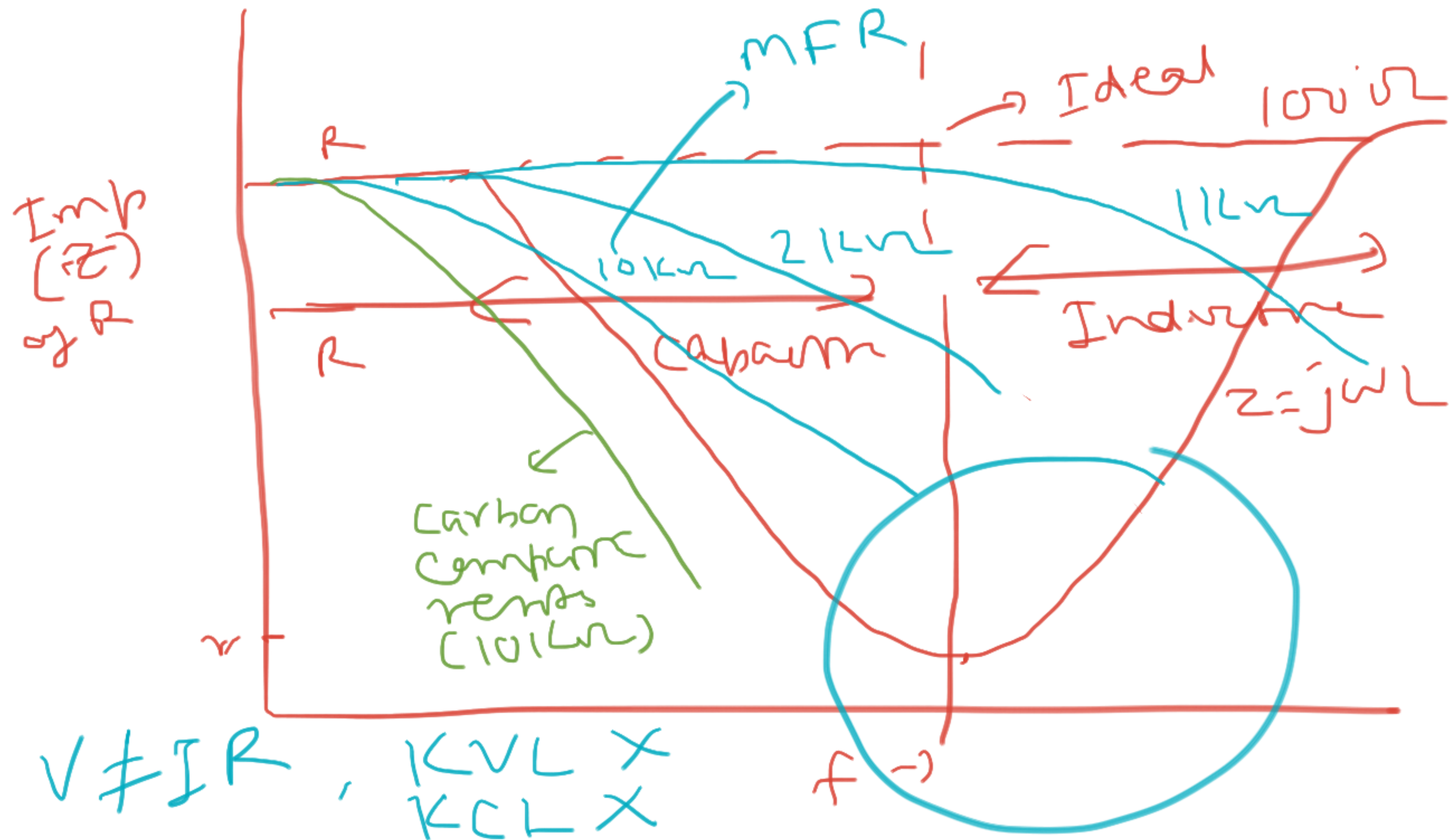

Capacitor : Dielectric constant

$$\epsilon_r = 1.000 \text{ (vacuum)}$$

$$= 1.01 \text{ (air)}$$


$$= 80 \text{ (water)}$$

charge retention capacity of medium


DC eqn circuit of Cap :




AC (RF) eqn ckt

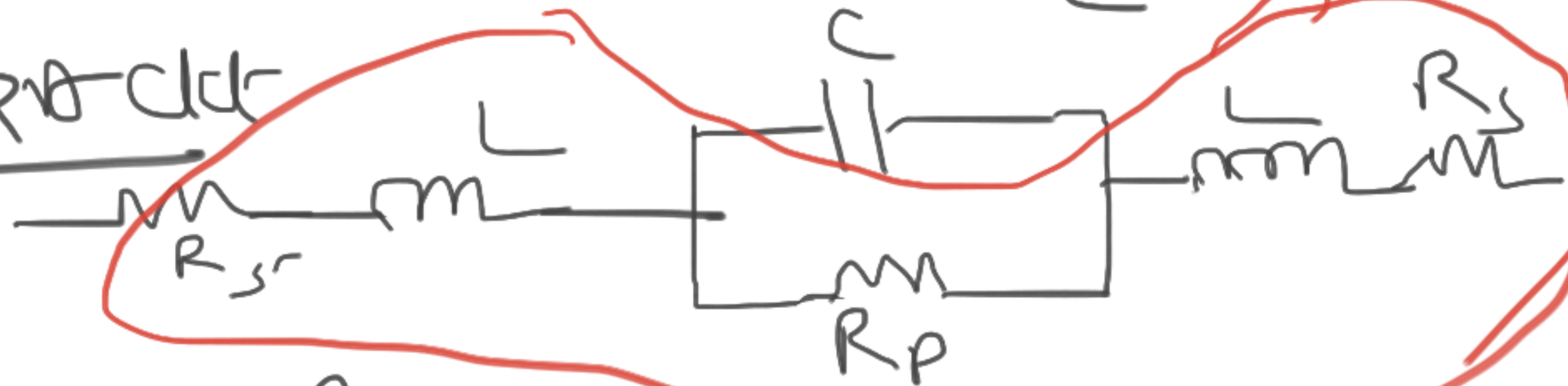

R_p = insulation resistance of cap

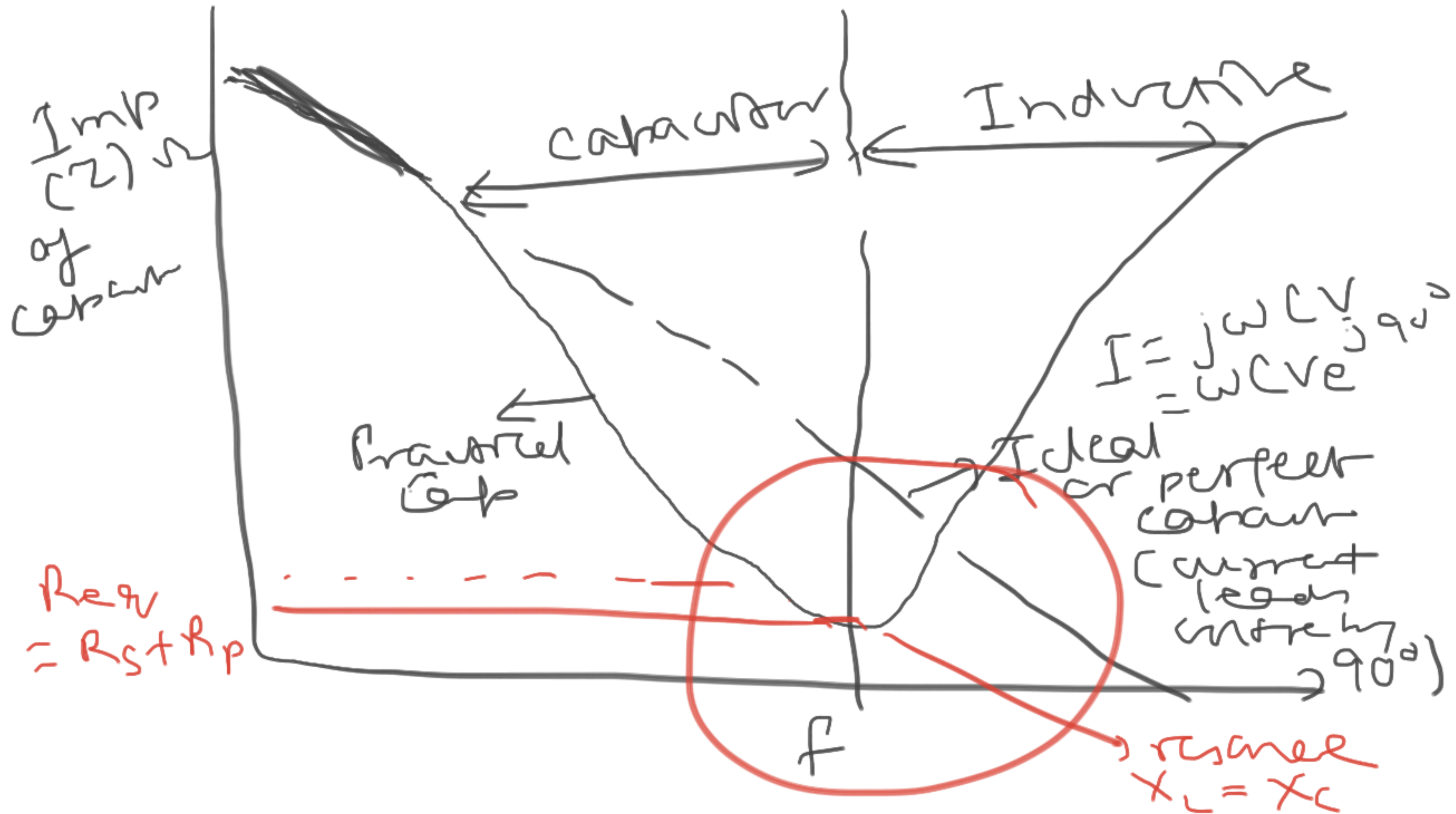
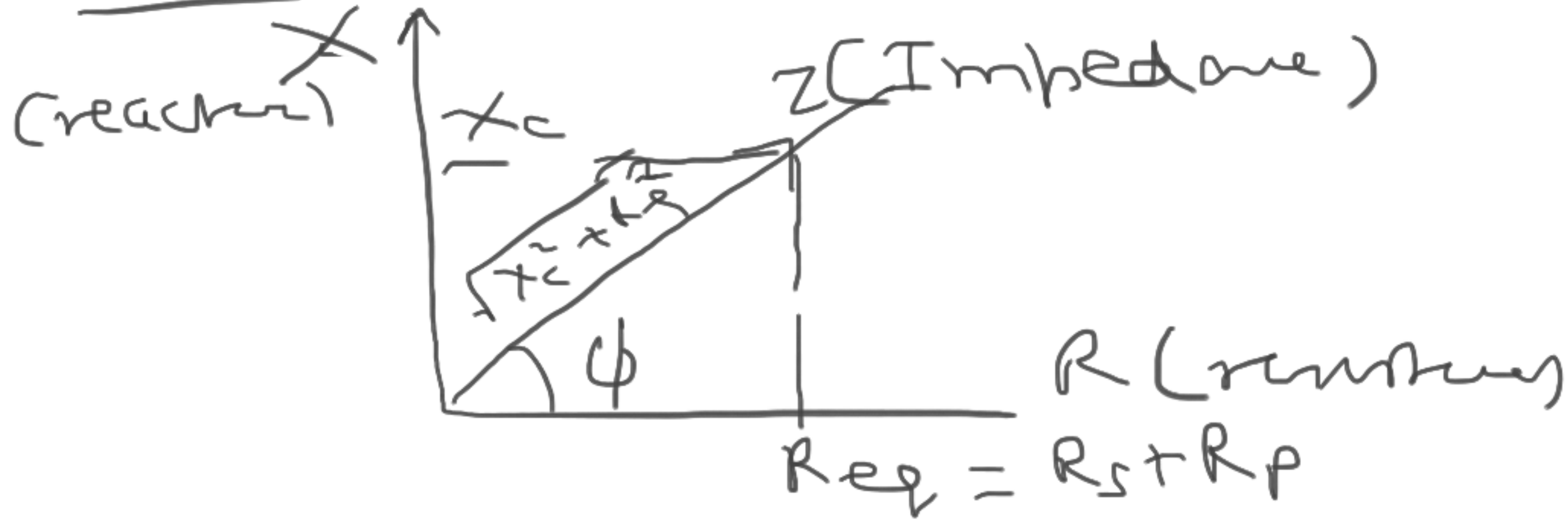
$$\underline{\text{Power factor (PF)} = \cos \phi}$$



$$PF = \cos \phi = \frac{R_{eq}}{\sqrt{X_c^2 + R_{eq}^2}}$$

usually, $R_{eq} < X_c$, $X_c = \frac{1}{\omega C}$

$\rightarrow \approx PF \approx \frac{R_{eq}}{X_c}$

ESR (equivalent series resistor)

↳ $R_{eq} = R_s + R_p$

Dissipation Factor (DF) → % of
ratio of ac resistance to reactance of
capacitor, $\Rightarrow DF = \frac{ESR \times 100\%}{X_c}$

$$= \frac{R_{eq} \times 100\%}{X_c}$$

Q-factor

$$Q = \frac{X_c}{R_{eq}} = \frac{1}{\omega C R_{eq}}$$

Loss tangent ($\tan \delta$)

↳ it is tangent of phase angle
relationship between cap voltage
& cap current

$$\tan \delta = \frac{\sigma}{\omega \epsilon}$$

σ = conductivity
 ϵ = permittivity

$$\epsilon = \epsilon_r + j \epsilon_{\text{imag}}$$

↓
dielectric
constant
(real)

$$\tan \delta = \frac{\epsilon_{\text{imag}}}{\epsilon_{\text{real}}}$$

$$Q = \frac{1}{\tan \delta}$$

For a perfect χ (ideal) cap

$$R_{eq} (\text{or } ESR) = 0$$

$$\Rightarrow PF = 0$$


$$\left(= \frac{R_p}{X_c} \right)$$

$$\Rightarrow Q = \infty$$

$$\left(= \frac{X_c}{R_p} \right)$$

Photolitho

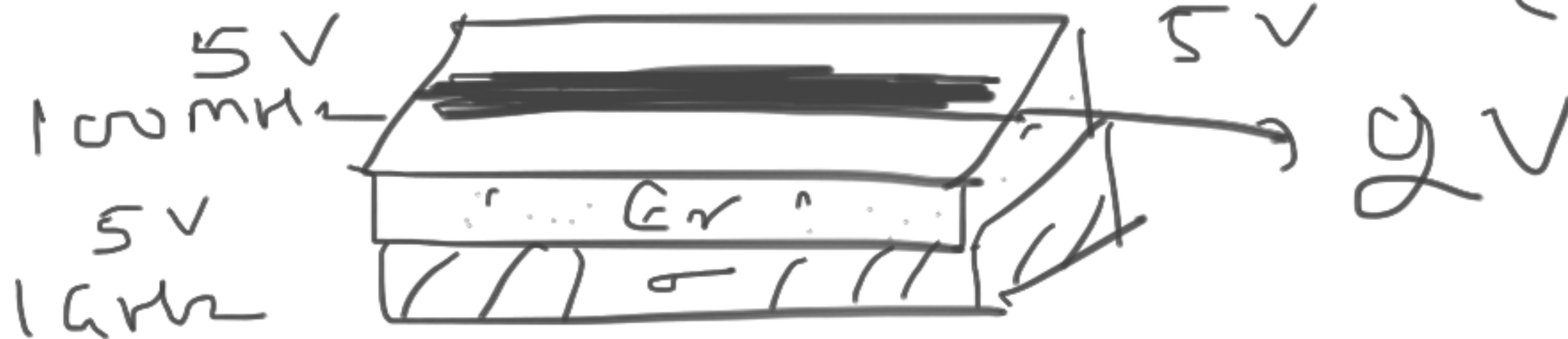PCB (FR-4) $\rightarrow E_r = 4$
 \hookrightarrow Reinforced fabric



$FeCl_3$
 (etchant)
 \downarrow
 eat away metal

Special PCBs \rightarrow Dielectric substrate
FR4, Arlon, Taconic

FR-4 $\Rightarrow \tan \delta = 0.0009$ at 100 MHz
 $= 0.09$ at 1 GHz

$\rightarrow \tan \delta = 0.0009$ at 1 GHz

apps. of comb

\rightarrow DC block

\rightarrow filter (L, C)

\rightarrow oscillator (L, C)