

25/03/2021

$$\gamma = \alpha + j\beta$$

α \downarrow (dB/m)
or (Np/m)

β \downarrow (rad/m)

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

(m^{-1})

$$Z_0 = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}}$$

(Ω)

$$v_p = \frac{\omega}{\beta}, \quad \omega = 2\pi f, \quad \beta = \frac{2\pi}{\lambda}$$

Case-1: Lossless line (Ideal) $\rightarrow R=0, G=0$

$$\therefore \gamma = \alpha + j\beta = j\omega\sqrt{LC} = 0 + j\omega\sqrt{LC}$$

$$\Rightarrow \boxed{\alpha = 0}; \quad \boxed{\beta = \omega\sqrt{LC}} \quad (\text{linear fun. of } \omega)$$

$$\therefore v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

$$Z_0 = R_0 + jX_0$$
$$\boxed{R_0 = \sqrt{\frac{L}{C}}, \quad X_0 = 0}$$

Case-2 :

Low loss line :

$$\begin{aligned} R &\ll \omega L \\ G &\ll \omega C \end{aligned}$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \sqrt{\left(1 + \frac{R}{j\omega L}\right) \left(1 + \frac{G}{j\omega C}\right) \cdot j\omega L \cdot j\omega C}$$

$$= j\omega \sqrt{LC} \left(1 + \frac{R}{j\omega L}\right)^{1/2} \left(1 + \frac{G}{j\omega C}\right)^{1/2}$$

$$= j\omega \sqrt{LC} \left[1 + \frac{R}{2j\omega L}\right] \left[1 + \frac{G}{2j\omega C}\right]$$

$$\left[\because (1+x)^n = 1 + nx + \dots \right]$$

$$\Rightarrow \gamma = \alpha + j\beta = j\omega \sqrt{LC} \left[1 + \frac{1}{2j\omega} \left(\frac{R}{L} + \frac{G}{C} \right) \right]$$

~~$\frac{RC}{\omega^2 LC}$~~ \rightarrow neglect because $\omega \ll \omega_c$

$$\approx j\omega \sqrt{LC} + \cancel{j\omega \sqrt{LC}} \frac{R}{2j\omega L} + \cancel{j\omega \sqrt{LC}} \frac{G}{2j\omega C}$$

$$\gamma = \alpha + j\beta = \underbrace{j\omega \sqrt{LC}}_{\beta} + \underbrace{\frac{1}{2} R \sqrt{\frac{C}{L}} + \frac{1}{2} G \sqrt{\frac{L}{C}}}_{\alpha \text{ (attenuation constant)}}$$

linear fun. of freq.

$$\sigma_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

$$Z_0 = R_0 + jX_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$= \sqrt{\frac{\frac{R}{j\omega L} + 1}{\frac{G}{j\omega C} + 1}} \cdot \frac{j\omega L}{j\omega C}$$

$$= \sqrt{\frac{L}{C}} \left(1 + \frac{R}{j\omega L}\right)^{1/2} \left(1 + \frac{G}{j\omega C}\right)^{-1/2}$$

$$Z_0 = \sqrt{\frac{L}{C}} \left[1 + \frac{1}{2j\omega} \left(\frac{R}{L} - \frac{G}{C}\right)\right]$$

$\left[(1+x)^n = 1 + nx + \dots\right]$ neglecting terms $\frac{-RS}{4j\omega^2 L} \because R \ll \omega L$

$$Z_o = \sqrt{\frac{L}{C}} \left[1 + \frac{1}{2j\omega} \left(\frac{R}{L} - \frac{C}{L} \right) \right]$$

$$= R_o + jX_o$$

$$\Rightarrow R_o = \sqrt{\frac{L}{C}}$$

$$\text{and } X_o = \sqrt{\frac{L}{C}} \cdot \frac{1}{2j\omega} \left(\frac{R}{L} - \frac{C}{L} \right) \approx 0$$

$$\left[\begin{array}{l} \because R \ll \omega L \\ \text{and } C \ll \omega C \end{array} \right]$$

case-3 : Distortionless line

losses of electric field = losses of magnetic field

\Rightarrow

$$R C = G L$$

\Rightarrow

$$\frac{R}{L} = \frac{G}{C}$$

$$\Rightarrow G = \frac{R C}{L}$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \sqrt{(R + j\omega L)\left(\frac{R C}{L} + j\omega C\right)}$$

$$= \sqrt{\frac{R^2 C}{L} + \omega^2 L C + j\omega R C + j\omega C R}$$

$$\gamma = \alpha + j\beta = \sqrt{\frac{R^2 C}{L} - \omega^2 LC + 2j\omega RC}$$

$$= \sqrt{\frac{C}{L} (R^2 - \omega^2 L^2 + 2j\omega RL)}$$

$$= \sqrt{\frac{C}{L} (R + j\omega L)^2}$$

$$\gamma = \alpha + j\beta = \sqrt{\frac{C}{L}} (R + j\omega L)$$

$$\Rightarrow \boxed{\alpha = R \sqrt{\frac{C}{L}} = R \sqrt{G}}$$

$$\left[\because G = \frac{R}{L} \right]$$

$$\boxed{\beta = \omega \sqrt{LC}}$$

$$\boxed{Q_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}}$$

$$Z_o = R_o + jX_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$



reactance

(+ve \Rightarrow inductive) $\rightarrow +jX_o$
 (-ve \Rightarrow capacitive) $\rightarrow -jX_o$

$$Z_o = \sqrt{\frac{R(1 + \frac{j\omega L}{R})}{G(1 + \frac{j\omega C}{G})}} = \sqrt{\frac{R}{G}} = \sqrt{\frac{L}{C}}$$

$$\left[\because G = \frac{R}{L} \right]$$

$$\Rightarrow Z_o = R_o + jX_o$$

$$\Rightarrow \left[\begin{aligned} R_o &= \sqrt{\frac{L}{C}} = \sqrt{\frac{R}{G}} \\ X_o &= 0 \end{aligned} \right]$$

Q: A 50 Ω distortionless line has
attenuation of 0.01 dB/m.
The line has capacitance of 0.1 nF/m
→ Find R , L & G of line $\rightarrow (C)$
→ " vel. of wave propagation
→ " loss if is 100 m long

Soln. $Z_0 = 50 \Omega$, $C = 0.1 \text{ nF/m} = 10^{-10} \text{ F/m}$
For distortionless line, $\left\{ \begin{array}{l} \frac{R}{L} = \frac{G}{C} \rightarrow (1) \\ R_0 = \sqrt{\frac{L}{C}} \rightarrow (2) \\ \alpha = R \sqrt{\frac{C}{L}} \rightarrow (3) \end{array} \right.$

3 eqns
3 unknowns (R, L, C)

$$\textcircled{2}: \sqrt{\frac{L}{C}} = 50 (= Z_0)$$

$$\textcircled{3}: R = \alpha \sqrt{\frac{L}{C}} = 0.057 \, \Omega/\text{m}$$

$$\textcircled{2}: L = CR_0^2 \approx 0.25 \times 10^{-6} \, \text{H/m}$$

$$\textcircled{1}: G = \frac{RC}{L} = 22.8 \times 10^{-6} \, \text{S/m}$$

$$= 22.8 \, \mu\text{S/m}$$

(S = mho = ohm⁻¹)

$$\rightarrow v_p = \frac{1}{\sqrt{LC}} = 2 \times 10^8 \, \text{m/sec}$$

$$\rightarrow \alpha = 0.01 \frac{\text{dB}}{\text{m}} \times 100 \, \text{m} = \underline{\underline{1 \, \text{dB}}}$$

Voltage Reflection Coefficient (Γ or ρ)

Lossless assumed ($\alpha = 0$)

$$\gamma = \alpha + j\beta \Rightarrow \underline{\gamma = j\beta}$$



Recall

⑨:

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

⑩:

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z}$$
$$= \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z}$$

($\because \gamma = j\beta$; $\frac{V_0^+}{Z_0} = I_0^+ = \frac{V_0^-}{Z_0} = I_0^-$)

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$

For lossless line ($\alpha = 0 \Rightarrow \gamma = j\beta$)

$$\textcircled{9}: V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z} \quad \textcircled{A}$$

$$\textcircled{10}: I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z} \quad \textcircled{B}$$

$$Z_L = \frac{V_L}{I_L}$$

Voltage V_L is voltage at load end (at $z=0$)

$$\therefore \textcircled{A}: V_L = V(z=0) = V_0^+ + V_0^-$$

$$\& \textcircled{B}: I_L = I(z=0) = \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0} = \frac{1}{Z_0} [V_0^+ - V_0^-]$$



$z = -l$

$z = 0$

source
or
generator
end

load
end

$$[e^{j\beta \cdot 0} = 1]$$

$$\therefore Z_L = \frac{V_L}{I_L} = \left(\frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right) Z_0$$

$$\Rightarrow V_0^- = \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) V_0^+$$

$$\Rightarrow \Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (\text{dimensionless})$$

ratio of amplitude (voltage)
of forward travelling wave
to that of reflected
(or backward travelling
wave)

(preferred)
over $\frac{I_0^-}{I_0^+}$

Since, $\frac{V_0^+}{I_0^+} = Z_0 = -\frac{V_0^-}{I_0^-}$ from (13)

$$\Rightarrow \frac{I_0^-}{I_0^+} = -\frac{V_0^-}{V_0^+} = -\Gamma$$

current reflection coefficient

Since, Z_L is a complex quantity,
 $Z_0 = 50 + j0$

Γ is a complex quantity, it can be
written as

$$\Gamma = |\Gamma| e^{j\theta_r} = |\Gamma| \angle \theta_r$$

magnitude of reflection coeff

angle of reflection coeff

Case-I: Matched line (perfect match)

$$\boxed{Z_L = Z_0}$$

→ desirable

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = 0$$

(no reflection)

Case-II:

↙ extreme

Short-circuited line

(shorted line)

$$\boxed{Z_L = 0}$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = -1 = 1 \angle \pi = 1 \angle 180^\circ$$

→ 100% reflection
a reversal of phase
of reflected wave

Case-III: Open-circuited line
extreme

$$Z_L = \infty$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = 1 = 1 \angle 0^\circ$$

→ 100% reflection
with no phase
change of reflected
wave

In general,

$$-1 < \Gamma < 1$$

or

$|\Gamma|$ is between 0 to 1
(0°) (100°)